

Device spacing on RS-485 buses

By Kevin Gingerich (Email: k-gingerich@ti.com)

High-Performance Linear/Interface

The RS-485 bus is a distributed parameter circuit whose electrical characteristics and responses are primarily defined by the distributed inductance and capacitance* along the physical media. The media is defined here as the interconnecting cable(s) or conducting paths, connectors, terminators, and RS-485 devices added along the bus. The following analysis derives a guideline for the amount of capacitance and its spacing that can be added to the bus.

For a starting approximation, the characteristic transmission line impedance at any cut point in the unloaded RS-485 bus is defined by the following equation, where L is the inductance per unit length and C is the capacitance per unit length.

$$Z = \sqrt{\frac{L}{C}}$$

As capacitance is added to the bus in the form of devices and their interconnections, the bus impedance is lowered to Z' , causing an impedance mismatch between the media and the loaded section of the bus.

As the input signal wave arrives at this mismatch in impedance, an attenuation (or amplification) of the signal will occur. The signal voltage at an impedance mismatch is $V_{L1} = V_{L0} + V_{J1} + V_{R1}$, where V_{L0} is the initial voltage, V_{J1} is the input signal voltage, and V_{R1} is the reflected voltage. The voltage reflected back from the mismatch is $V_{R1} = \rho_L \times V_{J1}$, where

$$\rho_L = \frac{Z' - Z}{Z' + Z}$$

and is the coefficient of reflection commonly used in transmission line analysis. The voltage equation can now be written as $V_{L1} = V_{L0} + V_{J1} + \rho_L \times V_{J1}$.

With fast transfer rates and electrically long** media, it becomes essential to achieve a valid input voltage level on the *first* signal transition from an output driver anywhere on the bus. This is called incident-wave switching. If incident-wave conditions are not achieved, reflected-wave switching must be used. To achieve a valid logic voltage level, reflected-wave switching depends upon reflected energy occurring some time after the first transition arrives.

* All capacitances are differential in this article. The differential is approximately one-half of the single-ended capacitance.

** "Electrically long" is defined here as

$$\tau > \frac{t_{10-90\%}}{3}$$

where τ is the one-way time delay across the bus and $t_{10-90\%}$ is the 10-to-90% transition time of the fastest driver output signal.

Assuming that the bus is terminated at both ends with the nominal media impedance and no fail-safe offset, an RS-485 driver will create a high-to-low voltage change from at least 1.5 V to -1.5 V, or a V_{J1} of -3 V. The signal voltage at the load, V_{L1} , should go below the minimum receiver input voltage threshold of -0.2 V.

$$-0.2 > 1.5 + (-3) + \rho_L \times (-3)$$

$$\rho_L > \frac{-0.2 - 1.5 + 3}{-3} = -0.43$$

Now we can solve for Z' :

$$\rho_L = \frac{Z' - Z_0}{Z' + Z_0} > -0.43$$

$$Z' - Z_0 > -0.43(Z' + Z_0)$$

$$Z'(1 + 0.43) > Z_0(1 - 0.43)$$

$$Z' > 0.4Z_0$$

If the loaded bus impedance is no less than $0.4Z_0$, the minimum threshold level should be achieved on the incident wave under all allowed cases.

What bus configuration rules should be used to keep the loaded bus impedance above $0.4Z_0$?

In the derivation of the minimum loaded-bus impedance, we treat the addition of devices and their capacitances in a distributed model. As such, the loaded-bus impedance can be approximated by


$$Z' = \sqrt{\frac{L}{C + C'}}$$

where C' is the added capacitance per unit length. If we knew the distributed inductance and capacitance of the media, we could calculate Z' directly. Unfortunately, manufacturers do not commonly specify these; but they generally do specify the characteristic impedance, Z_0 , and the capacitance per unit length, C . With these and the relationship

$$Z_0 = \sqrt{\frac{L}{C}}$$

we can solve for L , as $L = Z_0^2 C$. Then we can substitute into the equation for Z' and simplify:

$$Z' = \sqrt{\frac{Z_0^2 C}{C + C'}} = Z_0 \sqrt{\frac{C}{C + C'}}$$

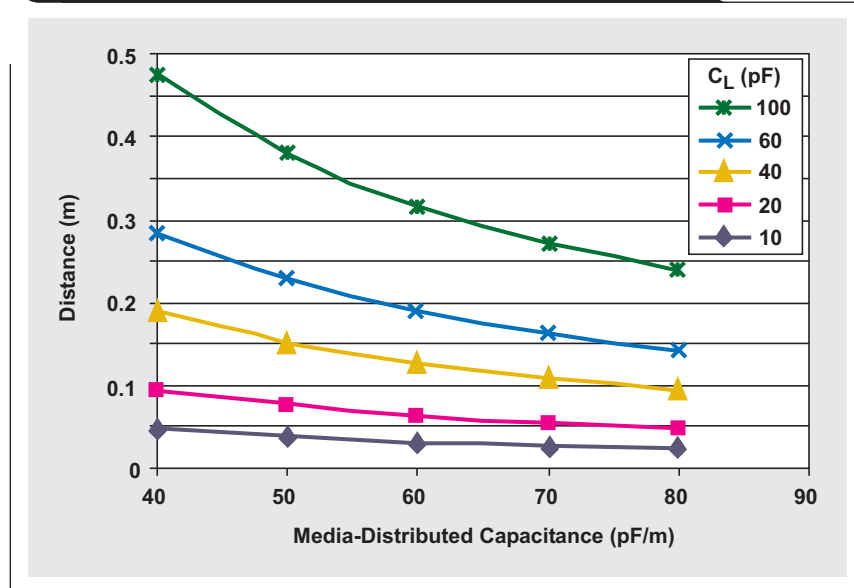Figure 1. Minimum RS-485 device spacing with device and media capacitance

C' is the distributed device capacitance (C_L) divided by the distance (d) between devices:

$$C' = \frac{C_L}{d}$$

Substituting this into the equation, we can solve for d :

$$Z' = Z_0 \sqrt{\frac{C}{C + \frac{C_L}{d}}}$$

$$\left(\frac{Z'}{Z_0}\right)^2 = \frac{C}{C + \frac{C_L}{d}}$$

$$C \left(\frac{Z_0}{Z'}\right)^2 = C + \frac{C_L}{d}$$

$$d = \frac{C_L}{C \left[\left(\frac{Z_0}{Z'}\right)^2 - 1 \right]}$$

Now substituting our minimum Z' of $0.4Z_0$ gives us d in meters (if C is pF/m) or feet (if C is pF/ft):

$$d > \frac{C_L}{C \left[\left(\frac{Z_0}{0.4Z_0}\right)^2 - 1 \right]}$$

$$d > \frac{C_L}{5.25C}$$

We now have a relationship for the minimum device spacing as a function of the distributed media and lumped-load capacitance. Figure 1 shows this relationship graphically.

Load capacitance includes contributions from the RS-485 line circuit bus pins, connector contacts, printed-circuit-board traces, protection devices, and any other physical connections as long as the distance from the bus to the transceiver is electrically short. RS-485 5-V transceivers, such as the SN65HVD1176, have a capacitance of 7 pF. Transceivers with a 3-V supply, such as the SN65HVD11, have about twice the capacitance that 5-V transceivers have at 16 pF. Board traces add about 0.5 to 0.8 pF/cm depending upon their construction. Connector and suppression device capacitance can vary widely. Media-distributed capacitance ranges from 40 pF/m for low-capacitance, unshielded, twisted-pair cable to 70 pF/m for backplanes.

This derivation gives guidelines for spacing of RS-485 nodes along a bus segment based upon the lumped-load capacitance. The method is equally applicable to other multi-point or multidrop buses, such as CAN, RS-422, or M-LVDS, with appropriate adaptation of the parameter values.

Related Web sites

interface.ti.com

www.ti.com/sc/device/SN65HVD11

www.ti.com/sc/device/SN65HVD1176

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 363 4824
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	180 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		Toll-Free Number
Australia	1-800-999-084	Malaysia	1-800-80-3973
China	800-820-8682	New Zealand	0800-446-934
Hong Kong	800-96-5941	Philippines	1-800-765-7404
India	+91-80-51381665 (Toll)	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Fax	+886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		
			ti-china@ti.com

C120905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2006 Texas Instruments Incorporated